

INTRODUCTION TO ELECTRICAL ENGINEERING (BESCK104B/ 204B)**MODULE-1**

Syllabus: Introduction: Conventional and non-conventional energy resources; General structure of electrical power systems using single line diagram approach. Power Generation: Hydel, Nuclear, Solar & wind power generation (Block Diagram approach).

DC Circuits: Ohm's Law and its limitations. KCL & KVL, series, parallel, series-parallel circuits. Simple Numerical.

INTRODUCTION**CONVENTIONAL & NON-CONVENTIONAL ENERGY RESOURCE**

Conventional Energy Resource Conventional energy sources are naturally present and have been in use for many years these are also known as non-renewable energy sources, which are present in a limited quantity and take over hundreds of years to form.

Ex: Coal, petroleum, firewood, fossil fuels, straw etc.

Non-Conventional Energy Resource

The Non-Conventional energy sources are the sources of energy which are used as the alternative of conventional energy sources. These are also known as renewable energy sources. Which are available abundance in nature and being regularly generated in short time. Ex: Solar, wind, tidal, biomass energy etc.

Difference between Conventional and Non-Conventional Energy Resource

Conventional Energy	Non-Conventional Energy
- The sources of energy that have been used all around the world for a long time are called conventional energy sources. - Conventional sources of energy available are limited quantity in nature. - Ex: coal, petroleum, natural gas, firewood, etc. - These sources are mainly used at large scale in commercial and industrial applications such in thermal power plants, fuel in vehicles, etc. - These are Non-renewable and are not pollution free.	- The energy sources whose evolution has been done the recent years are known as non- conventional energy sources. - Non-conventional sources are available in abundance in nature. - Ex: sun, wind, tides, water, biofuels, etc. - These sources are used at small scale in domestic and specific commercial and industrial applications such as solar power for houses, offices, etc. - These are renewable and pollution free

GENERAL STRUCTURE OF ELECTRICAL POWER SYSTEMS


The electrical power supply system consists of 3 divisions:

1. Generation
2. Transmission
3. Distribution

The power is generated in generating station. The transmission system is to deliver power from generating station to centres and to large industrial consumers. The distribution system is to deliver from centres to various consumers.

The single line diagram is as shown below

Single line diagram

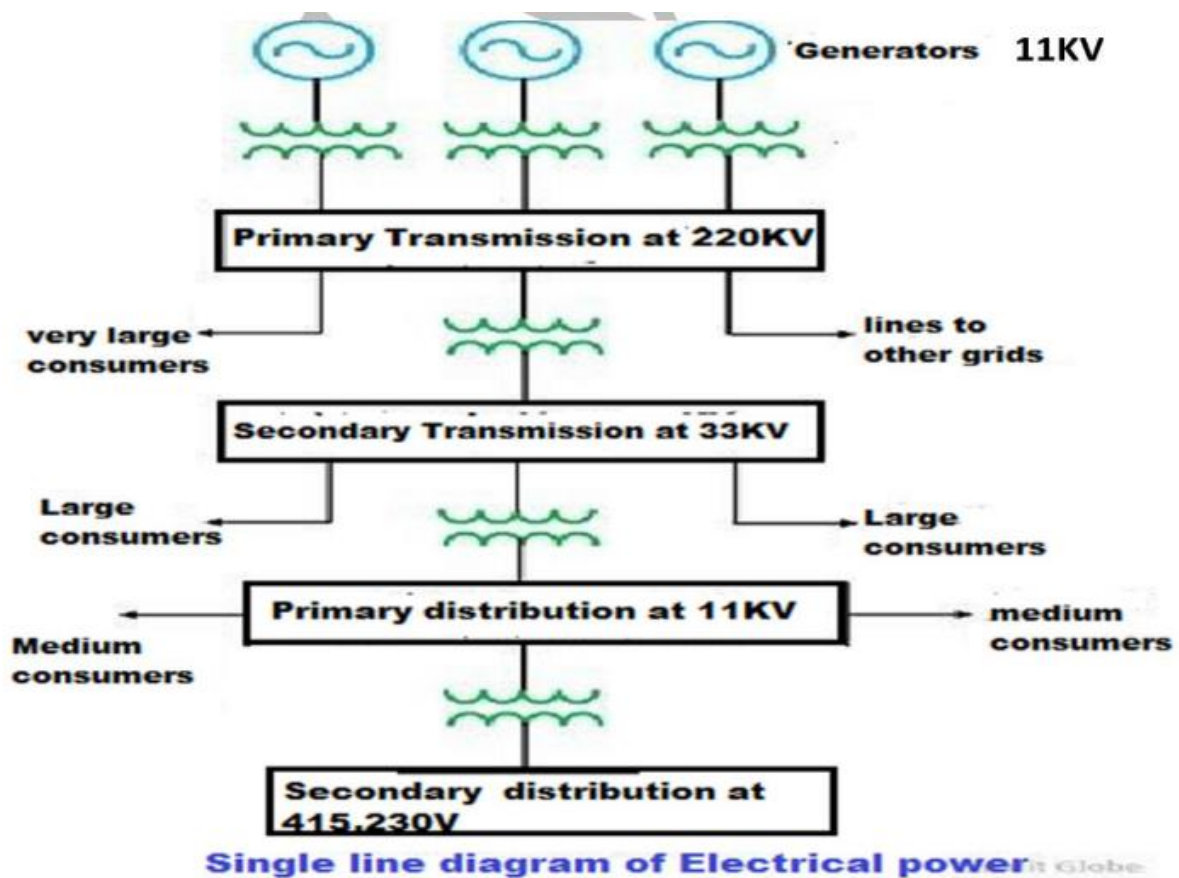


The block diagram and single line diagram is as shown in fig.1

- The electrical power is generated by alternators in generating stations.
- Usually the generated voltage is 11KV in certain cases 33KV also.
- In order to reduce the copper loss and for economy reasons the voltage is stepped up from 11KV to 220KV using step up transformers.
- The Primary transmission lines transmit the power from generating station to various substations.
- At this substation the voltage is step down from 220KV to 33KV by using step down transformer.
- Then the secondary transmission lines transmit the power to various substations and to large Industries.
- In primary distribution station the voltage is step down to 33KV to 11KV using step down Transformer.
- These substations transmit the power to various areas and to the medium scale industries.
- In each area using step down transformer the voltage is step down to 11K to 415V
- The most of domestic, commercial and small scale industries are supplied power at low voltage i.e 415V to 3-Phase load and 230V to single phase loads.


POWER GENERATION

Hydro power generation

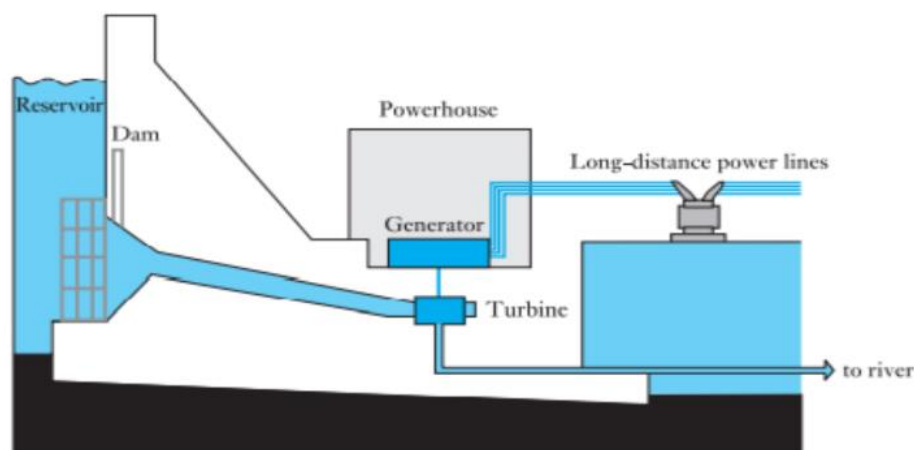Hydro power plants convert the potential energy of falling water into electricity. The block diagram of a hydro power station is as shown below.



General Layout of Hydro power plant

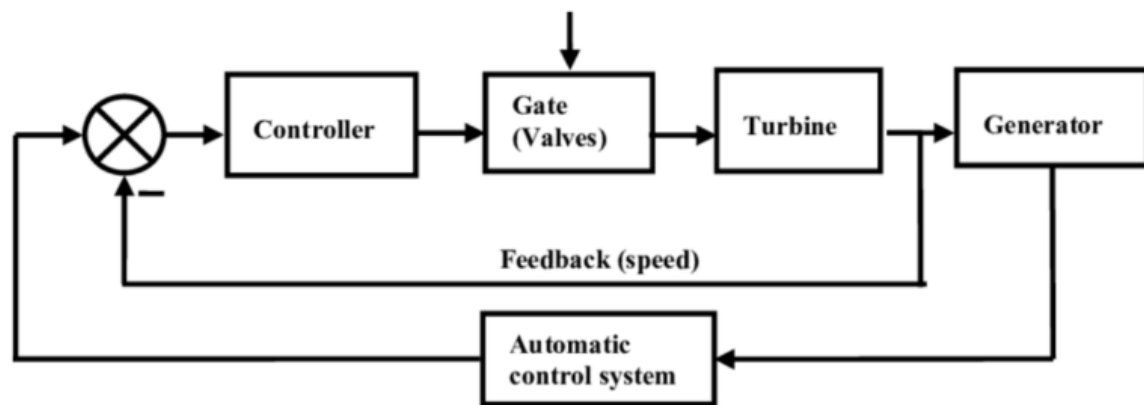


Block diagram of Hydro power plant


In Hydroelectric power stations the water can be store in a man-made lake, or reservoir. When water is released through the gates of reservoir, it spins a turbine which is placed below and water turbine captures the energy of the falling water. This turbine is coupled with the armature of an alternator which converts mechanical energy into electrical energy. The controller controls the flow of water so that the turbine rotates at constant speed. Hydroelectric power stations are becoming very popular because the reserves of fuels (i.e., coal and oil) are depleting day by day. They have the added importance for flood control, storage of water for irrigation and water for drinking purposes.

Nuclear power generation

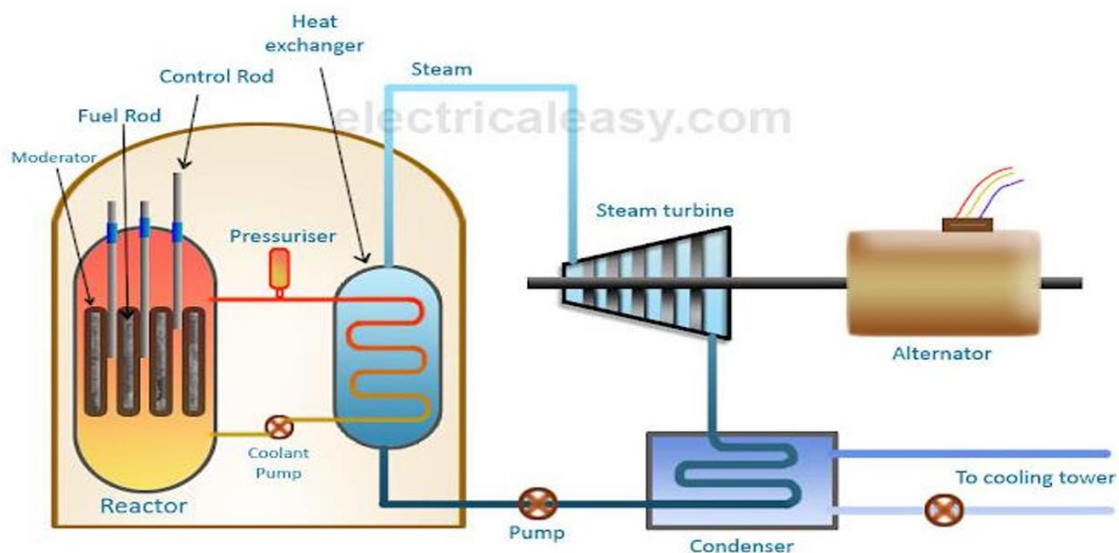Nuclear Power plants is a thermal power plant where heat generated by nuclear fission is used to drive the turbine. The block diagram is as shown below.



General Layout of Nuclear power plant

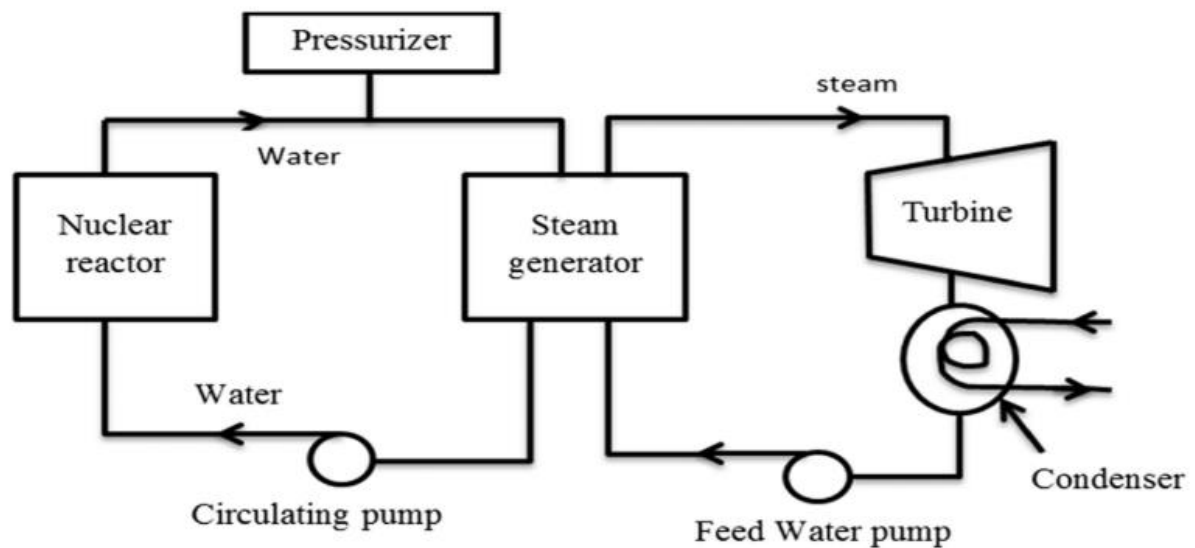


Block diagram of Nuclear power plant

Heavy elements such as Uranium (U^{235}) or Thorium (Th^{232}) are subjected to nuclear fission reaction in a nuclear reactor. Due to fission, a large amount of heat energy is produced which is transferred to the reactor coolant. The coolant may be water, gas or a liquid metal. The heated coolant is made to flow through a heat exchanger where water is converted into high-temperature steam. The generated steam is then allowed to drive a steam turbine. The steam, after doing its work, is converted back into the water and recycled to the heat exchanger. The steam turbine is coupled to an alternator which generates electricity. The generated electrical voltage is then stepped up using a transformer for the purpose of long distance transmission.

Wind power generation

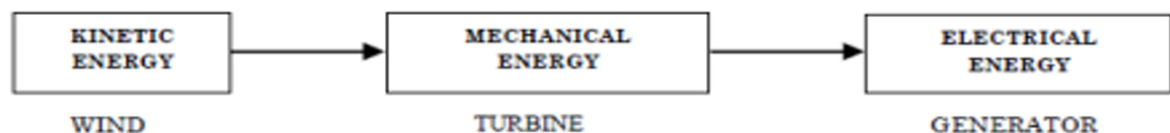In wind power generation the wind energy is used to generate electricity. The wind energy is converted into mechanical energy by an aero turbine. The block diagram is as shown below.



Wind energy system block diagram


The mechanical power is transferred through gears to the generator to increase its speed. Since rotor speeds are low, a gear system is necessary to match the synchronous speed of the generator. Due to fluctuations in wind speed, it not possible to obtain a power supply of a fixed

frequency from windmills. To overcome this problem, the output of generator is rectified and converted into AC with the help of inverter.

The Wind Energy Conversion System transfers kinetic energy from wind movement into mechanical energy with the help of a wind turbine. The generator shaft is connected to the wind turbine, and while the wind turbine rotates, the generator shaft rotates as well producing electrical energy.

Solar power generation

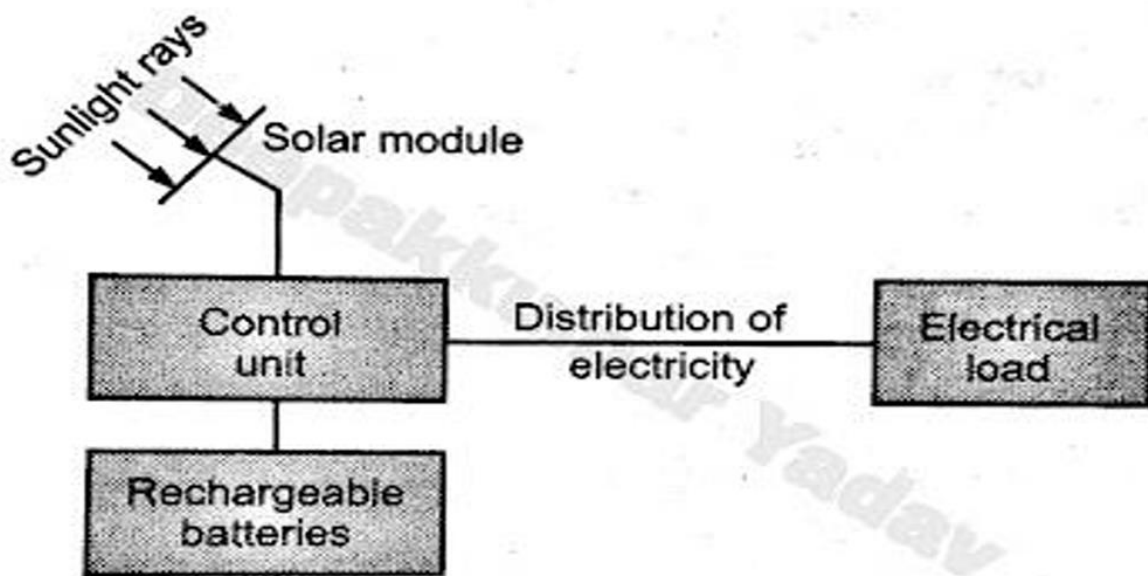In a Solar power plant the electricity is generated using photo voltaic system consists of PV array. The block diagram is as shown below



Basic Block Diagram of Photovoltaic System

The basic solar electric system consists of five parts namely solar module, rechargeable batteries, control unit, distribution of electricity and electrical load. Solar module is used to generate electricity from sunlight. When electricity is generated, the control unit will take part. Its function is to switch the loads manually or automatically, protect the batteries and wiring, monitor the performance of the system and give warnings when fault happens in the system. The rechargeable batteries are connected directly to the solar module. The rechargeable batteries are used to store electricity for later use at night and during cloudy periods. The distribution of electricity is direct current (DC) 12-24 V. It is much less dangerous than mains voltages, which is 100-240 V. Finally the generated electricity can be connected to the electrical load.

Ohm's Law

German physicist Georg Ohm derived relationship between voltage, current and resistance in an electrical circuit called ohm's law.

It states that "The potential difference applied across the circuit, is directly proportional current flowing through the circuit provided the temperature remains Constant ".

$$V \propto I$$

$$V = R I$$

R - Constant of proportionality called Resistance of a conductor in ohm's (Ω).

V – Potential difference across the circuit or voltage in volts (V).

I - Current in Amps (A).

Limitations of Ohm's law

- It is not applicable to non-metallic conductors like silicon carbide.
- It is not applicable to non-linear devices like diodes.
- It is not applicable to 'arc lamps', because arc produced exhibits non-linear characteristics.

Kirchhoff's Law

Kirchhoff's circuit laws are deals with the two parameters in the electric circuit - current and potential difference. They were first described in 1845 by German physicist Gustav Kirchhoff. He generalized the work of Georg Ohm.


i) Kirchhoff's Current Law (KCL)

Statement: It states that "The Algebraic sum of the currents meeting at a junction in an electric circuit is equal to zero."

$$\Sigma I = 0$$

Example: Consider a junction in an electrical network as shown in the fig. The currents I_1 and I_3 are taken as positive as they are entering the junction. While I_2 and I_4 are negative as leaving the junction.

Applying KCL to the above circuit

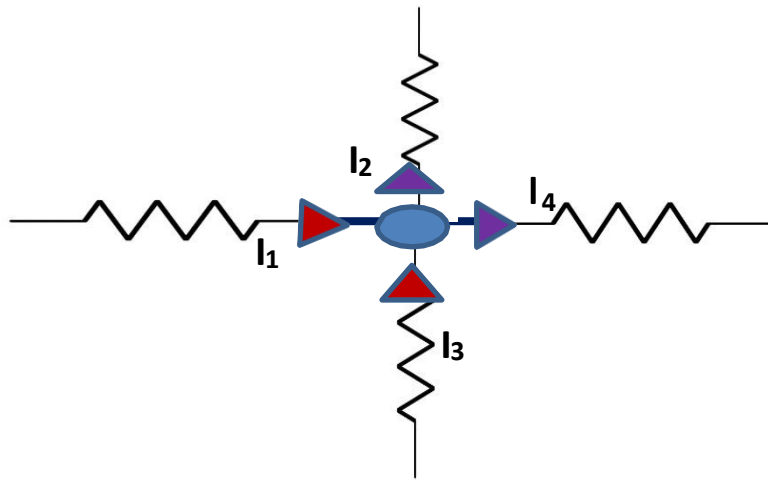

Applying KCL to the above circuit

$$I_1 - I_2 + I_3 - I_4 = 0$$

$$\text{I.e } I_1 + I_3 = I_2 + I_4$$

“The total current flowing towards a junction is equal to the total current leaving the junction.”


Note: Sign convention: The currents entering the junction taken as **positive** and the currents leaving the junction are taken as **negative**.

ii) Kirchhoff's Voltage law [KVL]

Statement: “In any closed path, the algebraic sum of the Emf's and the voltage drops across the circuit elements is equal to zero.”

$$\Sigma \text{Emf} + \Sigma \text{IR drops} = 0$$

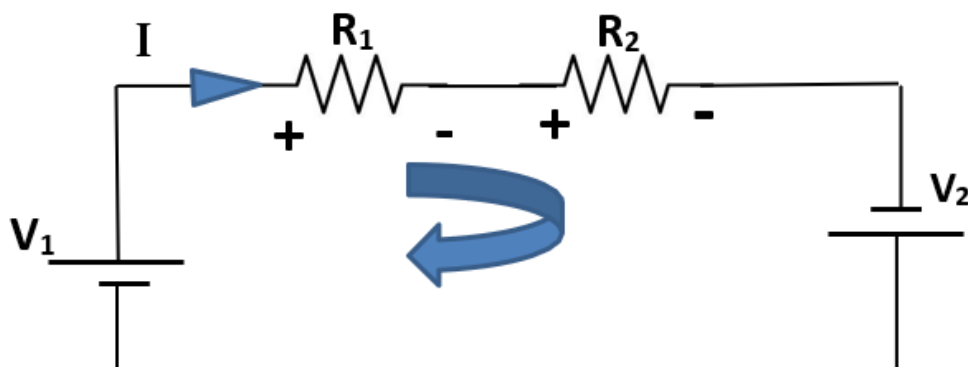Example: Consider an electrical network as shown in fig



Applying KVL to the loop

$$- IR_1 - IR_2 + V_2 + V_1 = 0$$

$$V_1 + V_2 = IR_1 + IR_2$$

Note: Sign convention: while tracing the path across

i) If its moving from „+“ to „-“, then it is voltage drop therefore take as **negative**.

ii) If its moving from „-“ to „+“, then it is voltage rise therefore take as **Positive**.

Electrical Power

The rate at which electrical work is done in a circuit is called **Electrical Power**.
Electrical power is denoted by P and measured in Watt (W).

$$P = VI$$

$$P = (IR) I = I^2 R \quad [V = IR]$$

$$P = V \left(\frac{V}{R} \right) = \frac{V^2}{R} \quad [I = V/R]$$

$$P = VI = I^2 R = \frac{V^2}{R} \text{ watts}$$

Energy

Energy is defined as the amount of electrical work is done in a circuit in a specified time.

It is denoted as „E“ and measured in Joules (J).


$$E = VI t = I^2 R t = \frac{V^2 t}{R} \text{ joules}$$

Analysis of Series and Parallel Circuits

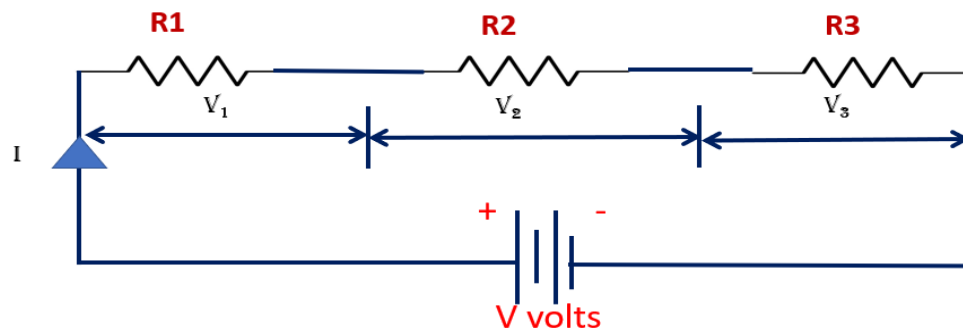I. Series Circuit

In a series circuit the finishing end of one resistor is connected to starting end of another resistor.

Consider three resistances connected series.



In series circuit the current flowing through all the resistances I same. Let „ I “ be the current flowing through all the resistors.

Let V_1 , V_2 , and V_3 be the voltages drops across the resistances R_1 , R_2 and R_3 respectively

The supply voltage V is the sum of the voltage drops across the resistances.

I.e $V = V_1 + V_2 + V_3$

According to Ohm's law

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

Applying Ohm's law to the overall circuit $V = I R_T$

R_T - is the Total or equivalent resistance of the circuit

$$V = V_1 + V_2 + V_3$$

$$I R_T = IR_1 + IR_2 + IR_3$$

$$I R_T = I [R_1 + R_2 + R_3]$$

$$R_T = R_1 + R_2 + R_3$$

Thus the Total or Equivalent Resistance in a series Circuit is equal to the Sum of the resistances connected in series.

Inference

- In Series circuit the same current is flowing through all resistances.
- The supply voltage **V** is the sum of the individual voltage drops across the each resistance.
- If **N** resistances connected in series then


$$R_T = R_1 + R_2 + R_3 + \dots + R_N$$

$$\text{and } V = V_1 + V_2 + \dots + V_N$$

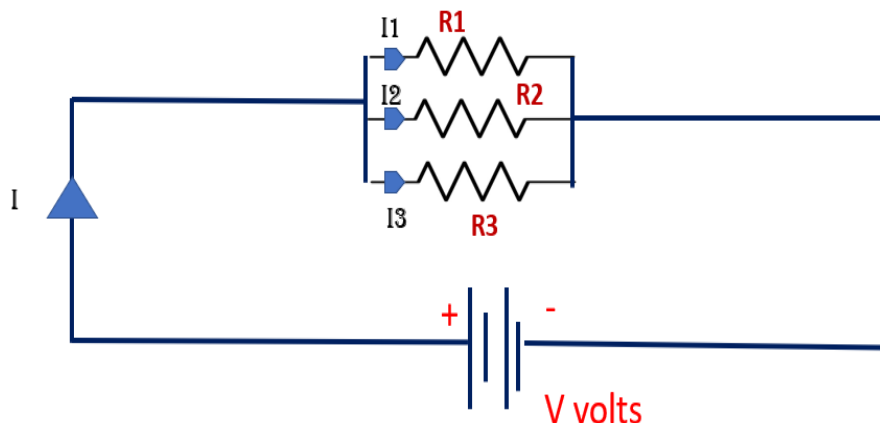I. Parallel Circuit

In a Parallel circuit the starting end of all the resistor are connected to one point and finishing end of all the resistors are connected to another point.

Consider three resistances connected in parallel.



In parallel circuit the voltage applied across each resistance is equal to the supply voltage.

Let **I** be the current drawn from the supply.

Let **I₁**, **I₂**, and **I₃** be the Current through the resistances **R₁**, **R₂** and **R₃**

respectively.

I.e

$$I = I_1 + I_2 + I_3$$

According to Ohm's law

$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

Applying Ohm's law to the overall circuit $I = \frac{V}{R_T}$

R_{eq} - is the Total or equivalent resistance of the circuit

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R_T} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\boxed{\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


Thus the reciprocal of Total or Equivalent Resistance in a parallel Circuit is equal to the Sum of the reciprocal of individual resistances connected in parallel.

Inference

- In Parallel circuit the voltage across each resistance is equal to supply voltage.
- The total current „I“ is the sum of the currents drawn by the each resistance.
- If „N“ resistances connected in parallel then

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \text{-----} + \frac{1}{R_N}$$

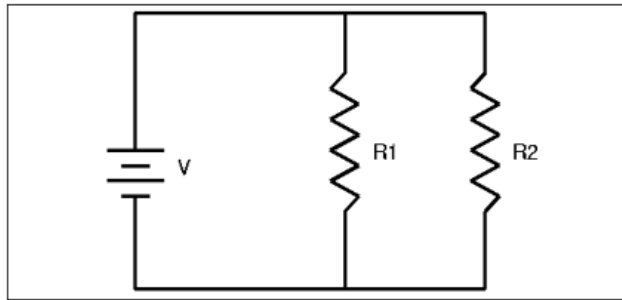Note: When 2 Resistances are connected in parallel then the Total resistance is




$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_T = \frac{R_1 + R_2}{R_1 R_2}$$

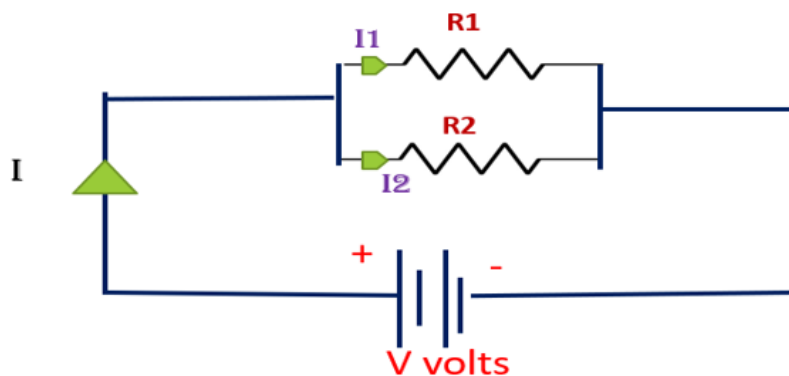III. Current Division in Parallel circuit of Resistors

Consider a parallel circuit of two resistors R_1 and R_2 connected across a supply Voltage of V Volts.



Let I_1 and I_2 be the Current through the resistances R_1 and R_2 respectively.

I.e $I = I_1 + I_2$ 1

According to Ohm's law

$$I_1 = \frac{V}{R_1} \quad \text{and} \quad I_2 = \frac{V}{R_2}$$

We know that in parallel circuit the voltage across each resistance is equal to

According to Ohm's law

$$I_1 = \frac{V}{R_1} \quad \text{and} \quad I_2 = \frac{V}{R_2}$$

We know that in parallel circuit the voltage across each resistance is equal to supply voltage.

$$\underline{\text{I.e}} \quad V = V_1 = V_2$$

Where V_1 and V_2 is the voltage across R_1 and R_2

$$\text{wkt } V_1 = I_1 R_1 \quad \text{and} \quad V_2 = I_2 R_2$$

$$\underline{\text{Therefore}} \quad I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{I_2 R_2}{R_1}$$

Substitute I_1 in equation 1 we get

$$I = I_1 + I_2$$

$$I = \frac{I_2 R_2}{R_1} + I_2$$

$$I = \underline{I_2} \left[\frac{R_2}{R_1} + 1 \right]$$

$$I = I_2 \left[\frac{R_2 + R_1}{R_1} \right]$$

Therefore

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

Similarly

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

List of Formulas

1. By ohm's Law $V=IR$, $I = \frac{V}{R}$, and $R = \frac{V}{I}$

2. In series Circuit $R_T = R_1 + R_2 + R_3 + \dots + R_N$

3. In Parallel circuit $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

If two resistances are in parallel $R_T = \frac{R_1 R_2}{R_1 + R_2}$

4. The current division in parallel circuit

$$\text{Current in a branch} = \frac{\text{Total current} \times \text{Resistance in an another branch}}{\text{sum of the resistances}}$$

I.e $I_1 = \frac{I R_2}{R_1 + R_2}$ and $I_2 = \frac{I R_1}{R_1 + R_2}$

5. Kirchhoff's Current Law (KCL) $\Sigma I = 0$

Total Sum of Incoming Currents = Total sum of outgoing Currents

6. Kirchhoff's Voltage law (KVL) $\Sigma \text{Emf} + \Sigma IR_{\text{drops}} = 0$


7. Electrical Power $P=VI = I^2 R = \frac{V^2 t}{R}$ watts

8. Energy $E=VI t = I^2 R t = \frac{V^2 t}{R}$ joules

Problems on DC circuits

1. A circuit consists of two parallel resistors having resistances of $20\ \Omega$ and $30\ \Omega$ respectively, connected in series with a $15\ \Omega$ resistor. If the current through $15\ \Omega$ resistor is 3A , find (i) the current in $20\ \Omega$ and $30\ \Omega$ resistors, (ii) the voltage across the whole circuit, (iii) voltage drop across $15\ \Omega$ resistor and (iv) the total power and power consumed in all resistors.

Solution:

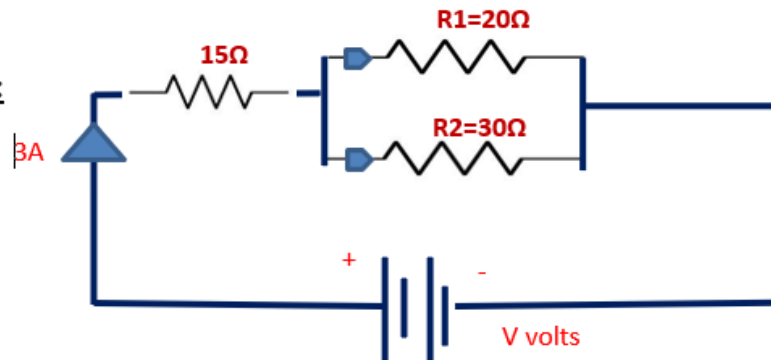

$$I_{20\Omega} = ? \quad I_{30\Omega} = ?$$

$$V = ? \quad V_{15\Omega} = ? \quad P = ?$$

$$P_{15\Omega} = ? \quad P_{20\Omega} = ? \quad P_{30\Omega} = ?$$

Current through the $15\ \Omega$ resistor $I_{15\Omega} = I = 3\text{A}$ the total current of the circuit

i) The current through $20\ \Omega$ is
$$I_{20\Omega} = \frac{IR_2}{R_1 + R_2}$$

$$I_{20\Omega} = \frac{3 \times 30}{30 + 20}$$

$$\boxed{I_{20\Omega} = 1.8\text{A}}$$

The current through $30\ \Omega$ is
$$I_{30\Omega} = \frac{I R_1}{R_1 + R_2}$$

$$I_{30\Omega} = \frac{3 \times 20}{30 + 20}$$

$$\boxed{I_{30\Omega} = 1.2\text{A}}$$

ii) Supply Voltage $V=?$

Wkt $V = I R_T$

$$R_T = \underline{(20 \parallel 30)} + 15$$

$$R_T = \frac{20 \times 30}{20+30} + 15$$

$$[R_p = \frac{R_1 R_2}{R_1 + R_2}]$$

$$R_T = 12 + 15 = 27 \Omega$$

Therefore

$$V = I R_T = 3 \times 27$$

$$V = 81 \text{ V}$$

iii) Voltage across 15Ω is $V_{15\Omega} =$ current flowing through the resistance $\times$ value of resistance

$$= 3 \times 15$$

$$V_{15\Omega} = 45 \text{ V}$$

iv) Power consumed by the circuit $P=?$

Power consumed by the 15Ω resistor $P_{15\Omega} = I_{15\Omega}^2 \times R$

$$= (3^2) \times 15 = 135 \text{ watts}$$

Power consumed by the 20Ω resistor $P_{20\Omega} = I_{20\Omega}^2 \times R$

$$= (1.8^2) \times 20 = 64.8 \text{ watts}$$

Power consumed by the 30Ω resistor $P_{30\Omega} = I_{30\Omega}^2 \times R$

$$= (1.2^2) \times 30 = 43.2 \text{ watts}$$


Total Power consumed by the circuit

$$P = 135 + 64.8 + 43.2 \quad \text{or} \quad P = VI = 81 \times 3$$

$$P = 243 \text{ Watts}$$

2. An 8-ohm resistor is in series with a parallel combination of two resistors 12 ohm and 6 ohms. If the voltage drop across 8ohm is 30V. find (i) the current in 12 Ω and 6 Ω resistors, (ii) the total power and power consumed by each resistor iii) Voltage drop across 6 Ω resistor iv) supply voltage .

Solution:

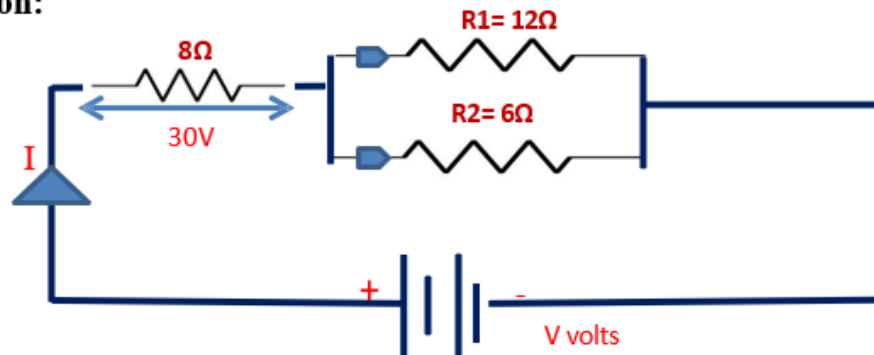

$$I_{12\Omega} = ? \quad I_{6\Omega} = ? \quad P = ?$$

Total or current through 8 Ω $I = V_{8\Omega} / R = 30 / 8$

$$I = 3.75 \text{ A}$$

$$\text{i) } I_{12\Omega} = \frac{I R_2}{R_1 + R_2} = \frac{3.75 \times 6}{12 + 6}$$

$$I_{12\Omega} = 1.25 \text{ A}$$

$$I_{6\Omega} = \frac{I R_1}{R_1 + R_2} = \frac{3.75 \times 12}{12 + 6}$$

$$I_{6\Omega} = 2.5 \text{ A}$$

- ii) Power consumed by the circuit $P = ?$

Power consumed by the 8 Ω resistor $P_{8\Omega} = I_{8\Omega}^2 \times R$

$$= (3.75^2) \times 8 = 112.5 \text{ watts}$$

Power consumed by the 12 Ω resistor $P_{12\Omega} = I_{12\Omega}^2 \times R$

$$= (1.25^2) \times 12 = 18.75 \text{ watts}$$

Power consumed by the 6 Ω resistor $P_{6\Omega} = I_{6\Omega}^2 \times R$

$$= 2.5^2 \times 6 = 37.5 \text{ watts}$$

Total Power consumed by the circuit

$$P = 112.5 + 18.75 + 37.5$$

$$\boxed{P = 168.75 \text{ Watts}}$$

iii) Voltage Drop across 6Ω resistor = $I_{6\Omega} \times R$

$$= 2.5 \times 6$$

$$\boxed{V_{6\Omega} = 15 \text{ V} = V_{12\Omega}}$$


iv) Supply or Total Voltage

$V =$ Voltage drop across 8Ω + Voltage drop across parallel combination

$$V = 30 + 15$$

$$\boxed{V = 45 \text{ V}}$$

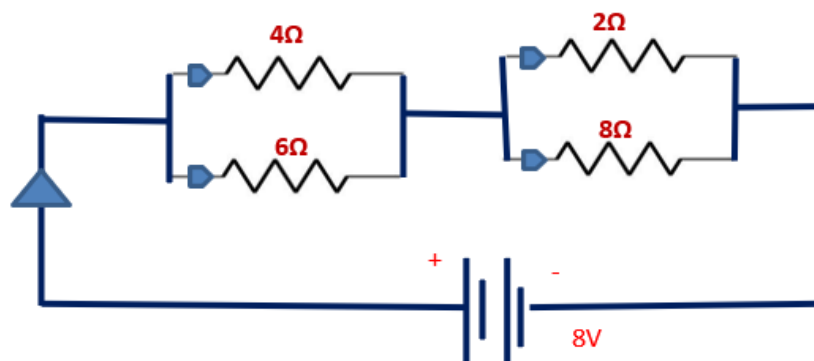3. For the circuit shown below find the current through all the resistances and the power consumed by the circuit



Solution: $I_{4\Omega}=?$ $I_{6\Omega}=?$ $I_{2\Omega}=?$ $I_{8\Omega}=?$ $P=?$

$$\text{Wkt } I = \frac{V}{R_{eq}}$$

$$R_T = (4 \parallel 6) + (2 \parallel 8) = \frac{4 \times 6}{4+6} + \frac{2 \times 8}{2+8} = 2.4 + 1.6 = 4 \Omega$$

$$R_T = 4 \Omega$$

$$I = \frac{V}{R_T} = \frac{8}{4} = 2 \text{ A}$$

$$\boxed{\text{Total current } I = 2 \text{ A}}$$

$$\text{Current in a branch} = \frac{\text{Total current} \times \text{Resistance in another branch}}{\text{sum of the resistances}}$$

$$I_{4\Omega} = \frac{2 \times 6}{4+6} = 1.2 \text{ A}$$

$$I_{6\Omega} = \frac{2 \times 4}{4+6} = 0.8 \text{ A}$$


$$I_{2\Omega} = \frac{2 \times 8}{8+2} = 1.6 \text{ A}$$

$$I_{8\Omega} = \frac{2 \times 2}{8+2} = 0.4 \text{ A}$$

ii) The power Consumed by the circuit $P = VI$
 $= 8 \times 2 = 16 \text{ watts}$

$P = 16 \text{ watts}$

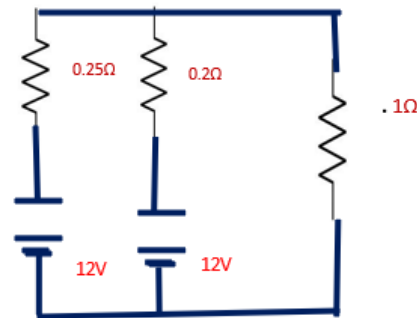5. The two 12V batteries with internal resistance of 0.2Ω and 0.25Ω respectively are joined parallel and resistance of 1Ω is placed across the terminals. Find the current supplied by the battery and power consumed by 1Ω resistor.



Solution:


Applying KVL to LOOP 1

$$-0.25I_1 + 0.2I_2 - 12 + 12 = 0$$

$$-0.25I_1 + 0.2I_2 = 0 \quad \text{--- (1)}$$

Applying KVL to LOOP 2

$$-1(I_1 + I_2) + 12 - 0.2I_2 = 0$$

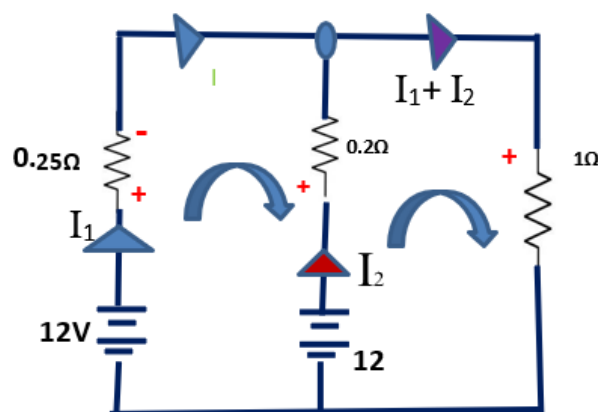

$$-I_1 - I_2 - 0.2 I_2 = -1$$

$$-I_1 - 1.2 I_2 = -12 \quad \text{---2}$$

Solving Equation 1 and 2

$$-0.25I_1 + 0.2I_2 = 0$$

$$-I_1 - 1.2 I_2 = -12$$

We get

$$\boxed{I_1 = 4.8A \text{ and } I_2 = 6A}$$


Therefore, current supplied from each battery is 4.8A and 6A

respectively Current through 1Ω resistor is $I_{1\Omega} = I_1 + I_2 = 4.8 + 6 =$


10.8A

Power consumed by 1Ω resistor is $P_{1\Omega} = I_{1\Omega}^2 \times R = 10.8^2 \times 1 = \mathbf{116.64watts}$

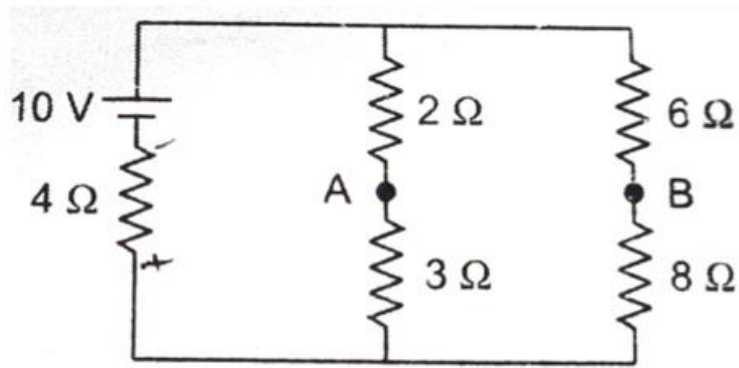7. Find current in the battery, the current in branch and pd (potential difference) across AB in the network shown.



Solution:

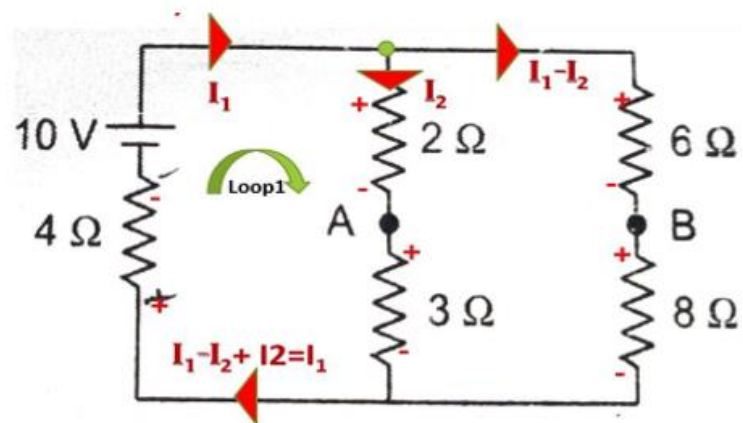

Applying KVL to LOOP 1

$$-2I_2 - 3I_2 - 4I_1 + 10 = 0$$

$$-4I_1 - 5I_2 = -10 \text{ ----- 1}$$

Applying KVL to LOOP 2

$$-6(I_1 - I_2) - 8(I_1 - I_2) + 3I_2 + 2I_2 = 0$$

$$-6I_1 + 6I_2 - 8I_1 + 8I_2 + 3I_2 + 2I_2 = 0$$

$$-14I_1 + 19I_2 = 0 \text{ ----- 2}$$

Solving Equation 1 and 2

$$-4I_1 - 5I_2 = -10$$


$$-14I_1 + 19I_2 = 0$$

Solving Equation 1 and 2

$$I_1 = 1.3\text{A}$$

$$I_2 = 0.95\text{A}$$

To find the pd across AB

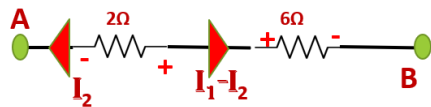


$$+2I_2 - 6(I_1 - I_2) = V_{AB}$$

$$V_{AB} = 2(0.95) - 6(1.3 - 0.95)$$


$$V_{AB} = -0.2\text{V}$$

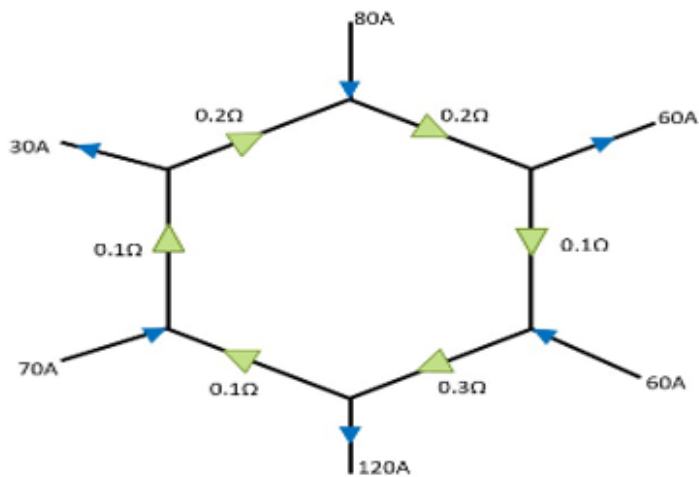▲ 14. Find the values of currents in all the branches of the network shown in figure



Solution:

Let I be the current flowing from A to B

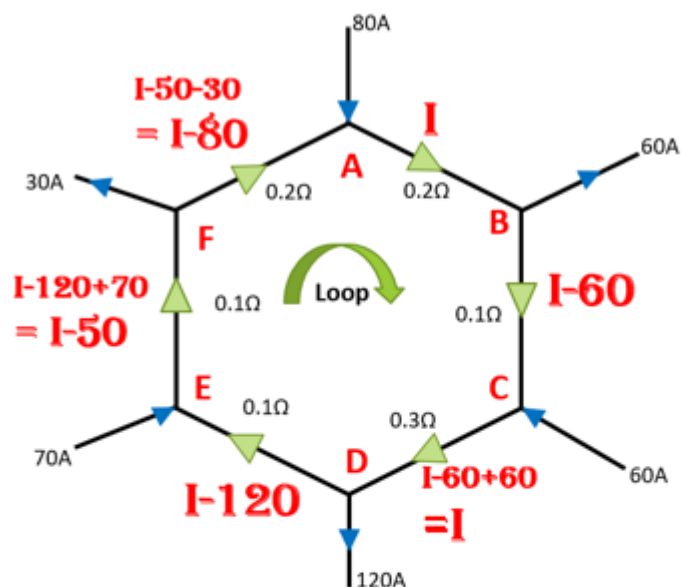

Applying KVL to LOOP ABCDEFA

$$-0.2I - 0.1(I-60) - 0.3I - 0.1(I-120)$$

$$-0.1(I-50) - 0.2(I-80) = 0$$

$$-0.2I - 0.1I + 6 - 0.3I - 0.1I$$

$$+12 - 0.1I + 5 - 0.2I + 16 = 0$$

$$-1I = -39A$$

$$I = 39A$$

Current in Branch AB is $I = 39A$

Current in Branch BC is $I - 60 = 39 - 60 = -21A$


Current in Branch CD is $I = 39A$

Current in Branch DE is $I - 120 = 39 - 120 = -81A$


Current in Branch EF is $I - 50 = 39 - 50 = -11A$

Current in Branch FA is $I - 80 = 39 - 80 = -41A$

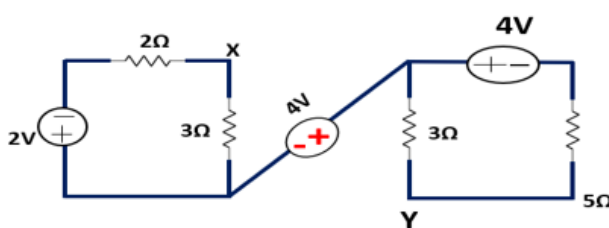15. Obtain the potential difference V_{xy} in the circuit shown



Solution:

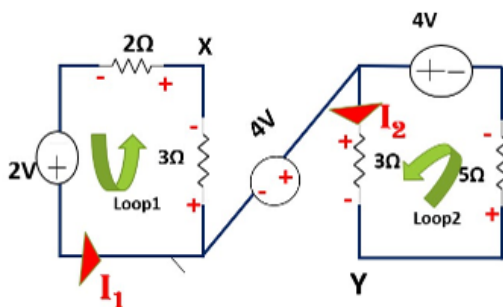

Applying KVL to LOOP1

$$-3I_1 - 2I_1 + 2 = 0$$

$$-5I_1 = -2$$

$$I_1 = -2/-5 = 0.4A$$

Applying KVL to LOOP2

$$-3I_2 - 5I_2 + 4 = 0$$

$$-8I_2 = -4$$

$$I_2 = -4 / -8 = 0.5 \text{ A}$$

To find the pd across XY



$$3I_1 + 4 - 3I_2 = V_{xy}$$

$$V_{xy} = 3(0.4) + 4 - 3(0.5)$$

$$V_{xy} = 3.7 \text{ V}$$